

Reg. No.

--	--	--	--	--	--	--	--	--	--

B.E. / B.TECH. DEGREE EXAMINATIONS, DEC 2019
 Fifth Semester
EC16503 – TRANSMISSION LINES AND WAVE GUIDES
(Electronics and Communication Engineering)
(Regulation 2016)

Time: Three Hours

Maximum : 100 Marks

Answer ALL questions

PART A - (10 X 2 = 20 Marks)

		CO	RBT
1.	Find the characteristic impedance of a line at 1000 Hz if $Z_{oc} = 650 \angle -30^\circ \Omega$ and $Z_{sc} = 300 \angle 70^\circ \Omega$.	1	U
2.	Sketch the equivalent circuit of a unit length of transmission line.	1	R
3.	Write the expression for the input impedance of open and short circuited dissipation less line.	1	R
4.	Express standing wave ratio in terms of reflection co-efficient.	1	R
5.	Why shorted circuited stub is preferred to open circuited stub?	2	U
6.	A 75Ω lossless transmission line is to be matched to a resistive load impedance of $Z_L = 100\Omega$ via a quarter wave section. Calculate the characteristic impedance of the quarter-wave transformer.	2	AP
7.	Mention the condition for pass band and stop band of a filter.	3	R
8.	Compare constant-K and m-derived filters.	3	U
9.	Which is the dominant mode of a rectangular wave guide? Why?	4	U
10.	Mention the applications of resonant cavities.	4	R

PART B - (5 X16 = 80 Marks)

11. (a) (i) Derive the general solution of a transmission line. (10) 1 R
 (ii) A transmission has the following constants $R= 10.4\Omega$, $L= 3.666mH$, $C= 0.00835\mu F$ and $G= 0.08\mu mhos$. Calculate its characteristic impedance, attenuation, phase constant and phase velocity. (6) 1 AP

(OR)

- (b) (i) Discuss the theory of open and short circuited lines with voltage and current distribution diagrams and also derive the input impedance expression. (10) 1 U
 (ii) A low loss transmission line of 100 ohms characteristic impedance is connected to a load of 200 ohm. Calculate the reflection co-efficient and the standing wave ratio. (6) 1 AP

12. (a) (i) Explain and derive an expression for the input impedance of a dissipationless line and also find the input impedance is maximum and minimum at a distance 's'. **(10)** **1** **U**
- (ii) Discuss the various parameters of the open wire and coaxial line at high frequencies. **(6)** **1** **R**

(OR)

- (b) (i) Briefly explain on: **(4 + 4)** **1** **R**
- (1) Standing waves
- (2) Reflection loss
- (ii) Describe an experimental set up for the determination of VSWR and wavelength of RF line. **(8)** **1** **R**
13. (a) Explain the technique of single stub matching and derive the length and location of the stub with suitable diagram. **(16)** **2** **U**

(OR)

- (b) (i) A 75Ω transmission line is connected to a load impedance of $150 + j225\Omega$ at 500MHz. Find the position and length of a short circuited stub required to match the line using smith chart. **(10)** **2** **AN**
- (ii) Explain the significance of smith chart and its application in transmission lines. **(6)** **2** **U**
14. (a) (i) Draw and explain the design and operation of constant-K T-section bandpass filter with necessary equations and diagrams. **(8)** **3** **U**
- (ii) Design constant-K T-section bandpass filter for the cutoff frequencies 2KHz and 6KHz and the design impedance is 500Ω . **(8)** **3** **AP**

(OR)

- (b) Derive and draw the m-derived T and π section for low pass and high pass filter. **(16)** **3** **R**
15. (a) Derive the expression for the field strengths for TE wave between a pair of parallel perfectly conducting planes of infinite extent in the X and Y directions. The plates are separated in Z direction by 'a' meter. **(16)** **4** **AP**

(OR)

- (b) Explain the propagation of electromagnetic waves in a cylindrical waveguide with suitable expressions. **(16)** **4** **U**