

Reg. No.

--	--	--	--	--	--	--	--	--	--

B.E. / B.TECH. DEGREE EXAMINATIONS, DEC 2019

Fourth Semester

EE16403 – Digital Logic Circuits
(Electrical and Electronics Engineering)
(Regulation 2016)

Time: Three Hours

Maximum : 100 Marks

Answer ALL questions

PART A - (10 X 2 = 20 Marks)

	CO	RBT
1. Simplify $f = (b + bc)(b + b'c)(b+d)$.	1	AP
2. Construct an OR gate using universal NAND gates.	1	AP
3. Sketch the logic diagram of 8 : 3 encoder circuit.	2	AP
4. Realize a half adder using VHDL coding.	2	AP
5. State the truth table of JK flip flop and T flip flop.	3	R
6. Estimate the type of Mod counters used to display minutes in digital clock.	3	AN
7. What is flow table and primitive flow table?	3	R
8. Compare sequential and combinational circuits.	3	U
9. Develop a simple Inverter logic using NPN Transistor.	5	AP
10. Define Fan-out and Fan-in.	5	R

PART B - (5 X16 = 80 Marks)

11. (a) (i) Simplify the Boolean function using map method and implement using universal gates	(8)	1	AP
$F(w,x,y,z) = \sum m(1,3,5,6,7,8,12,14) + d(9,15)$			
(ii) Reduce the following expression using K-map and implement using logic gates.	(8)	1	AP
$f = x'y'z + w'xz + wxy' + wxz + w'xyz$			
(OR)			
(b) (i) State and prove Demorgan's theorem.	(6)	1	U
(ii) List various binary codes used in digital systems and explain any two binary codes with suitable illustrations.	(10)	1	U
12. (a) (i) Design and implement using logic gates 4-bit Gray to Binary code converter.	(8)	2	AN
(ii) Design a full subtractor circuit with three inputs A, B, C and two outputs D and B. Implement the circuit using universal gates.	(8)	2	AN
(OR)			
(b) (i) Design a 4 bit even parity generator.	(8)	2	AN

- (ii) Implement the following Boolean function using 8:1 Multiplexer (8) 2 AP

$$F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$$

13. (a) Draw the state diagram from the present state – Next state table given. Also, apply state minimization technique to reduce the number of states in the following: (16) 3 AP


Present state	Next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

(OR)

- (b) Design MOD 10 synchronous counter using JK flip flop. (16) 3 AN
14. (a) (i) Explain in detail the cycles and races in asynchronous sequential design circuit. (10) 3 U
- (ii) Design a hazard free circuit for the given Boolean function (6) 3 AN
- $$F = \sum m(1,3,6,7,13,15)$$

(OR)

 - (b) Analyse the given synchronous sequential circuit and obtain its state diagram (16) 3 AN



15. (a) Derive the PLA programming table for the boolean function combinational circuit. Minimize the number of product terms and implement using PLA programming device. (16) 4 AP

$$F1 = \sum m(0,1,2,3,4,7,8,11,12,15)$$

$$F2 = \sum m(2,3,6,7,8,9,12,13)$$

$$F3 = \sum m(1,3,7,8,11,12,15)$$

$$F4 = \sum m(0,1,4,8,11,12,15)$$

(OR)

- (b) Enumerate the different logic families used to fabricate digital gate ICs. Draw and Explain the NOR / OR Logic using Emitter Coupled Logic. (16) 5 U