

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2023**  
 Third Semester  
**CS18201 – DIGITAL PRINCIPLES AND SYSTEM DESIGN**  
*(Computer Science and Engineering)*  
**(Regulation 2018/2018A)**

**TIME: 3 HOURS**

**MAX. MARKS: 100**

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Students will be able to learn the different types of number systems and simplification of Boolean functions.	2
CO 2	Students will be able to understand various logic gates and their usage.	3
CO 3	Students will be able to study, analyse and design various combinational circuits and its implementation using VHDL.	4
CO 4	Students will be able to study, analyse and design various synchronous and asynchronous sequential circuits and its implementation using VHDL.	4
CO 5	Students will be able to understand the different type of memory and their structures.	4

**PART- A (10 x 2 = 20 Marks)**  
 (Answer all Questions)

	CO	RBT LEVEL
1. Convert (1,3215) to binary.	1	2
2. List the characteristics of grey code.	1	2
3. Draw the circuit of half subtractor.	2	2
4. Define De- multiplexing.	2	2
5. Draw the characteristic ' table of SR Latch.	3	2
6. Compare Sequential and combinational circuit.	3	3
7. What is the use of primitive flow table.	4	2
8. What is a Cycle?	4	2
9. List the different types of ROM.	5	2
10. List the operations performed in a memory.	5	2

**PART- B (5 x 14 = 70 Marks)**

	Marks	CO	RBT LEVEL
11. (a) Construct the given using only NOR gates $F(a,b,c,d) = \text{Pi} (1,3,4,5,7,9,11,13,14)$	(14)	1	4

**(OR)**

(b)	Simplify using K Map method $F(A,B,C,D,E) = (0,2,5,7,9,11,15,17,18,20,24,25,30,31) + d(1,4,10,13,14,,21,25)$	(14)	1	4
12. (a)	Design a BCD to Excess3 code convertor. <b>(OR)</b>	(14)	2	3
(b)	Design a multiplexer circuit for the boolean function $F(A,B,C,D) = (1,3,4,5,7,8,,11, 14,15)$	(14)	2	3
13. (a)	Explain in detail about the various types of shift register. <b>(OR)</b>	(14)	3	4
(b)	With a neat diagram explain the working of a 4 bit ring counter.	(14)	3	4
14. (a)	Discuss in detail about the various hazards that exists in a digital system. <b>(OR)</b>	(14)	4	3
(b)	Design a gated latch circuit with two inputs $G$ (gate) and $D$ (data), and one output $Q$ . Binary information present at the $D$ input is transferred to the $Q$ output when $G=1$ . The $Q$ output will follow the $D$ input as long as $G=1$ . When $G$ goes to 0, the information that was present at the $D$ input at the time the transition occurred is retained at the $Q$ output.	( )	4	3
15. (a)	Discuss in detail about the various error detection and correcting codes. <b>(OR)</b>	(14)	5	3
(b)	Implement the following Boolean functions using PLA: $F1(A,B,C) = (01,2,4)$	(14)	5	3
<b><u>PART- C (1 x 10 = 10 Marks)</u></b> (Q.No.16 is compulsory)				
		Marks	CO	RBT LEVEL
16.	Design and implement a 3-bit synchronous counter.	(10)	2	5

\*\*\*\*\*