
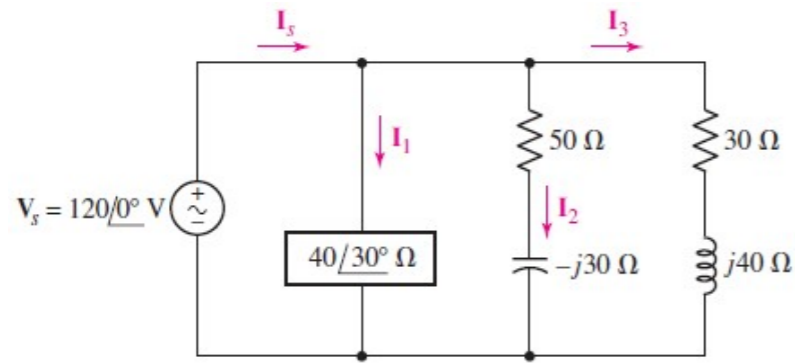


(14) 4 3

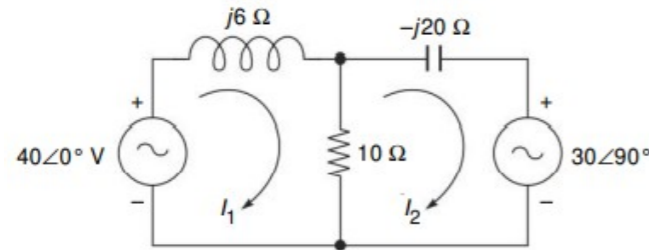


(OR)

(b) For the given circuit, find the complex power delivered by all the voltage sources. (14) 2 3



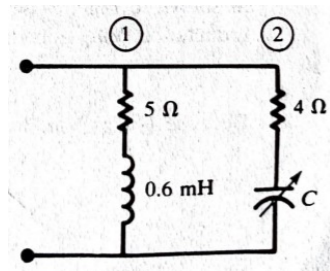
13. (a) (i) Determine the value(s) of C for which the circuit shown is resonant at 5000 rad/s. (10) 3 3




(ii) A RLC series circuit consists of R=16Ω, L=2mH and C=2μF. Calculate resonant frequency and Quality factor. (4) 3 3

(OR)

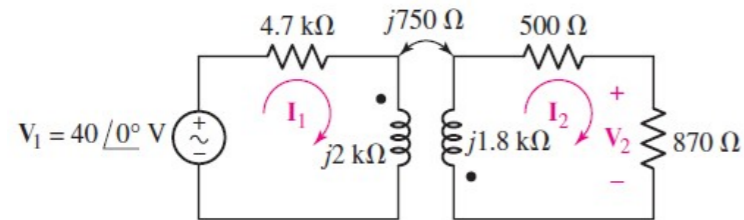(b) For the given circuit, determine the mesh current I₁ and I₂. (14) 3 3




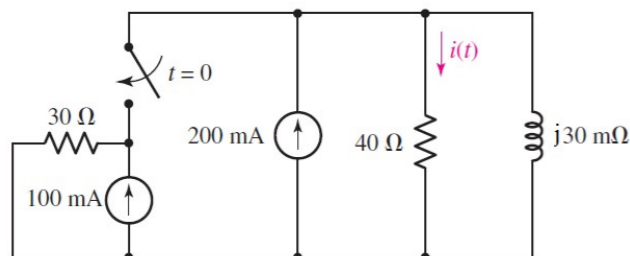14. (a) Obtain an expression for *i(t)* as labeled in the circuit diagram, and determine the power dissipated in the 40Ω resistor at *t* = 2.5 ms. (14) 4 3




(OR)

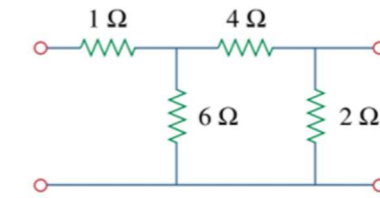(b) Determine the admittance parameters for the given circuit.




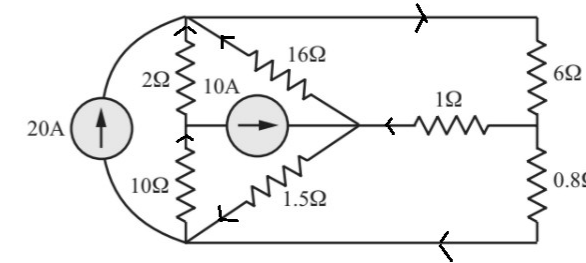15. (a) For the given network, obtain the incidence matrix (A) and cut-set matrix (C). Also, express the branch voltages in terms of twig voltages. (14) 5 3



(OR)

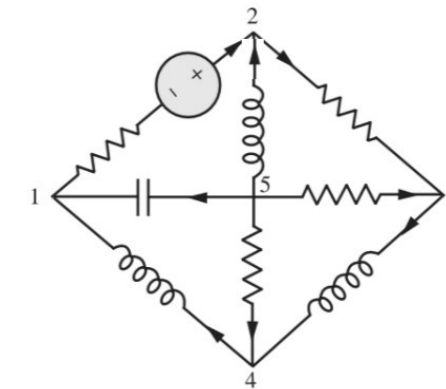(b) (i) For the given network, determine the incidence matrix (A) and Tie-set matrix (B). Also, express branch currents in terms of loop currents. (14) 5 3



PART- C (1 x 10 = 10 Marks)

(Q.No.16 is compulsory)

Marks CO RBT LEVEL

16. With regard to the circuit represented below, determine (a) *i_L(0-)*; (b) *i_R(0-)*; (c) *v_C(0-)*; (d) *v_C(0+)*. (10) 4 3

