

Reg. No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2023**

First Semester

**EE18152 – BASIC ELECTRICAL ENGINEERING**

(Electronics and Communication Engineering)

(Regulation 2018/2018A)

TIME: 3 HOURS

MAX. MARKS: 100


COURSE OUTCOMES	STATEMENT
CO 1	Apply various circuit analysis technique to solve problems in DC and AC Circuits.
CO 2	Apply various network reduction technique and network theorem to solve problems in DC and AC Circuits.
CO 3	Illustrate the construction, working principle, characteristics and applications of Transformer and Separately excited DC Motor.
CO 4	Illustrate the construction, working principle, characteristics and applications of Induction motor and Synchronous Generator.
CO 5	Explore the significance of the Electrical Installation and different power converter.

**PART- A (10 x 2 = 20 Marks)**

(Answer all Questions)

CO RBT LEVEL

1 2

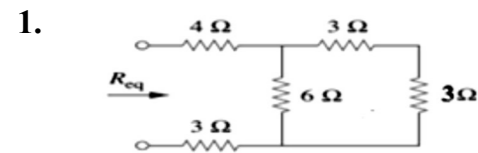

Solve the given circuit to determine Req.


- |     |  |   |   |
|-----|--|---|---|
| 2.  | Summarize the formulas required for converting delta network to star network.            | 1 | 2 |
| 3.  | What are the limitations of Reciprocity theorem?   | 2 | 2 |
| 4.  | State Thevenin Theorem and draw its equivalent circuit.                                  | 2 | 1 |
| 5.  | Outline the assumptions considered for an ideal transformer.                             | 3 | 2 |
| 6.  | Justify why the induced emf in a dc motor is called back or counter emf.                 | 3 | 3 |
| 7.  | How will you find the speed of an ac machine with given frequency and poles. Justify it? | 4 | 2 |
| 8.  | Why Single Phase Induction Motor is not Self Starting?                                   | 4 | 2 |
| 9.  | Distinguish MCB and MCCB   | 5 | 2 |
| 10. | Sketch the circuit diagram of buck converter and boost converter.                        | 5 | 2 |

**PART- B (5 x 14 = 70 Marks)**

Marks CO RBT LEVEL

(14) 1 3


11. (a)

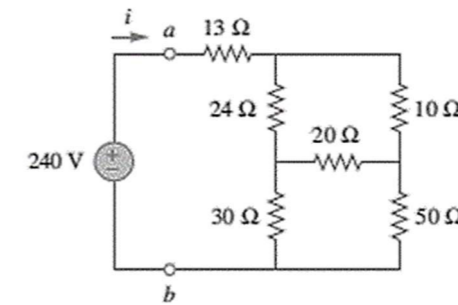

Calculate the value of current i flowing in the circuit shown.

(OR)


(b)

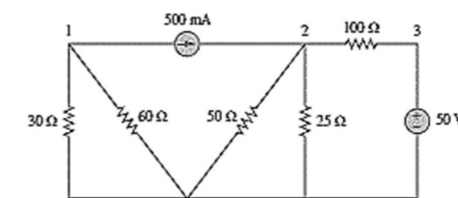

Calculate the nodal voltages in the circuit shown.

(14) 1 3

12. (a)

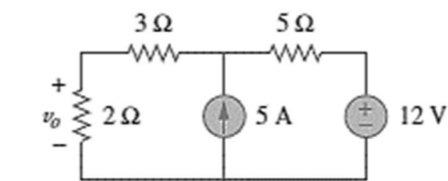


Using superposition theorem, calculate v<sub>o</sub> in the circuit shown.

(14) 2 4

(OR)

(b)

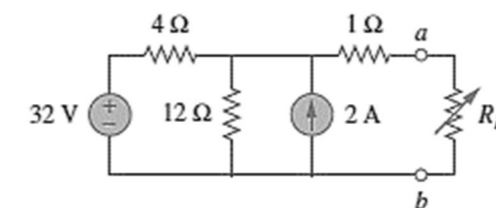

Find the Thevenin equivalent circuit across a-b and find the current through the load resistor R<sub>L</sub>=16Ω.

(14) 2 4

13. (a)

A single phase 50-Hz transformer has 20 primary turns and 200 secondary turns. If the primary winding is connected to a 230V supply, calculate (i) The value of maximum core flux (ii) The voltage induced in the secondary winding (iii) the primary current when the secondary current is 13A.

(14) 3 3

(OR)

(b) Derive the equation relating back-emf and speed of dc motor and discuss the speed control method used separately excited dc motor. (14) 3 3

14. (a) (i) Draw a typical torque-slip characteristics curve of 3-phase induction motor and deduce the condition for maximum torque. (8) 4 3

(ii) Show that the three-phase currents flowing in three phase windings generate a rotating magnetic field. (6) 4 3

(OR)

(b) (i) Explain construction and working principle of Synchronous Generator. (7) 4 3

(ii) Discuss the various types of losses that can occur in an induction motor. Identify the loss that impact motor efficiency. (7) 4 3

15. (a) Draw the circuit diagram of a buck boost converter and explain its operation with equivalent circuit for different modes and waveforms (14) 5 3


(OR)

(b) Briefly explain the components of LT Switchgear and its types. (14) 5 3

**PART- C (1 x 10 = 10 Marks)**  
(Q.No.16 is compulsory)

Marks	CO	RBT LEVEL
(10)	1	5

16.

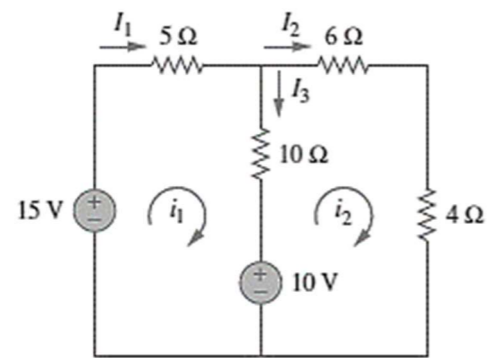

For the circuit shown, calculate the branch currents  $I_1$ ,  $I_2$ , and  $I_3$  using mesh analysis.

\*\*\*\*\*