

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E / B.TECH.DEGREE EXAMINATION, MAY 2023

Third Semester

EE18201 – ELECTRIC CIRCUIT ANALYSIS

(Electrical and Electronics Engineering)

(Regulation 2018 /Regulation2018A)

TIME:3 HOURS

MAX. MARKS: 100

- CO1 Analyze DC and single phase AC electrical circuits
- CO2 Simplify DC and AC electrical circuits using network theorems
- CO3 Study resonance phenomenon in electrical circuits and understand the effect of magnetic coupling between windings
- CO4 Perform transient analysis of electrical circuits and model circuits as 2 port networks
- CO5 Analyze three phase AC electrical circuits

PART- A(10x2=20Marks)

(Answer all Questions)

	CO	RBT LEVEL
1. An Electric iron is rated 1000W, 230V. Find the current drawn and resistance of the heating element.	1	2
2. Distinguish between a Loop and Mesh in a circuit	1	2
3. State maximum power transfer theorem	2	1
4. State the steps to solve the super position theorem.	2	2
5. Define Apparent power and Power factor.	3	1
6. What is parallel resonance?	3	2
7. Write down the time constants of R-L and R-C circuit.	4	1
8. When is a two port network is said to be reciprocal?	4	2
9. Distinguish between unbalanced supply and unbalanced load.	5	2
10. If active power of 3 phase motor is 5600W and Power factor is 0.81 Find its reactive power.	5	3

PART- B(5x 14=70Marks)

Marks CO RBT
LEVEL

11. (a) Determine the total current flowing through the circuit as shown in figure 1. (14) 1 3

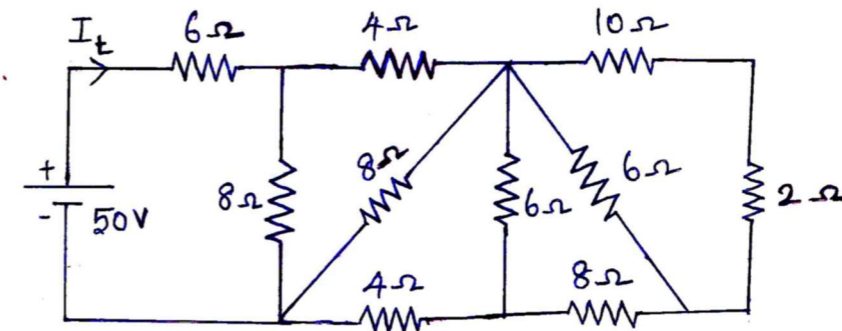


Figure 1.

(OR)

- (b) Determine the current I_2 of the given Figure 2 using mesh analysis (14) 1 3 technique. Also, apply nodal analysis method to verify the current I_2 value.

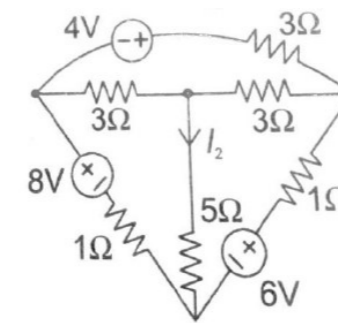


Figure 2.

12. (a) What are the limitations of superposition theorem? With suitable circuit example state and prove the superposition theorem. (14) 2 4

(OR)

- (b) Determine the Thevenin's equivalent across the terminal A and B of the circuit shown in figure 3. (14) 2 4

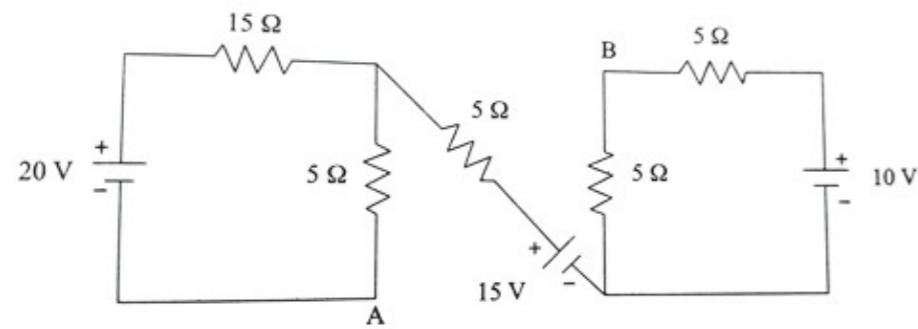


Figure 3.

PART- C(1x 10=10Marks)

(Q.No.16 is compulsory)

Marks	CO	RBT LEVEL
(10)	5	4

16. A 3 phase, 400V supply is given to a delta connected load of impedances $10\angle 30^\circ\Omega$, $10\angle 45^\circ\Omega$ and $2.5\angle 60^\circ\Omega$ respectively in each branch. Find the line currents and draw the phasor diagram.

13. (a) Determine the value of R_L of a network comprising $(R_L + j20)\Omega$ and $(20 - j10)\Omega$ connected in parallel operated at resonance condition. (14) 3 3

(OR)

- (b) Derive the expression for the equivalent inductance of (i) series opposing and (ii) series aiding circuits. (14) 3 3

14. (a) Derive the DC response of RL and RC series circuits. Compare their performances. (14) 4 3

(OR)

- (b) A series RLC circuit with $R=20\Omega$, $L=0.05\text{ H}$ and $C=20\mu\text{F}$ is excited from a voltage source of $V=100\text{ V}$. Obtain the equation for current in the circuit. (14) 4 3

15. (a) A 3-phase 4-wire 400 V supply is given to balanced star connected load of impedance $(8+6j)\Omega$ in each branch. Determine line current, power factor and total power. (14) 5 4

(OR)

- (b) Show that three phase power can be measured by two watt meters. Draw the phasor diagrams. Derive an expression for power factor in terms of wattmeter readings. (14) 5 4