

Reg. No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B. E / B. TECH.DEGREE EXAMINATION, MAY 2023**

Fifth Semester

**EE18501 – POWER SYSTEM ANALYSIS**

(Electrical and Electronics Engineering)

(Regulation 2018)

TIME:3 HOURS

MAX. MARKS: 100

- CO1 Develop the equivalent model of power system and construct the admittance and impedance matrices.
- CO2 Formulate the steady-state power flow problem and apply numerical solution algorithms for analysis.
- CO3 Compute short circuit capacity (SCC) of power system using matrix building algorithm under balanced fault.
- CO4 Compute short circuit capacity (SCC) of power system using symmetrical components under various faults.
- CO5 Formulate power system stability problem under large disturbance and apply numerical solution algorithms for analysis.

**PART- A(10x2=20Marks)**

(Answer all Questions)

- |  | CO | RBT LEVEL |
|--|----|-----------|
| 1. Represent a transformer with off nominal tap ratio into its $\pi$ -model equivalent circuit.  | 1  | 3         |
| 2. Write the expression to determine new elements of Y-bus matrix after eliminating $n^{\text{th}}$ node using Kron's reduction technique.   | 1  | 3         |
| 3. Why one of the buses is taken as slack bus in power system?   | 2  | 2         |
| 4. What is the best value of acceleration factor in Gauss-Seidel load flow solution method? Why is it necessary?   | 2  | 2         |
| 5. The positive sequence impedance of a 2-bus system is $j \begin{bmatrix} 0.15 & 0.20 \\ 0.10 & 0.30 \end{bmatrix} p.u.$ Find the fault current when symmetrical fault occurs at bus 2. | 3  | 3         |
| 6. Synchronous impedance is more than transient reactance – Justify.   | 3  | 4         |
| 7. If the phase currents are $I_a = 2 + j3$ , $I_b = 0$ and $I_c = -3 + j4$ Amp in a 3-phase, 4-wire system. Determine the current through the neutral.                                  | 4  | 3         |
| 8. Why the neutral grounding impedance $Z_n$ appears as $3Z_n$ in the zero sequence network?   | 4  | 4         |
| 9. What is small signal stability and how it is analyzed?  | 5  | 4         |
| 10. Write the expression for stiffness coefficient of synchronous machine.   | 5  | 4         |

**PART- B (5x 14=70Marks)**

Marks CO RBT LEVEL

11. (a) Draw the reactance diagram for the power system shown in Figure 1. Neglect resistance and use a base of 100 MVA, 220 kV in  $50\Omega$  line. The ratings of the generator, motor and transformer are given below.  
 Generator: 40 MVA, 25 kV,  $X''=20\%$   
 Synchronous motor: 50 MVA, 11 kV,  $X''=15\%$   
 Y-Y Transformer: 40 MVA, 33/220 kV,  $X=15\%$   
 Y-  $\Delta$  Transformer: 30 MVA, 11/220 kV ( $\Delta/Y$ ),  $X=15\%$

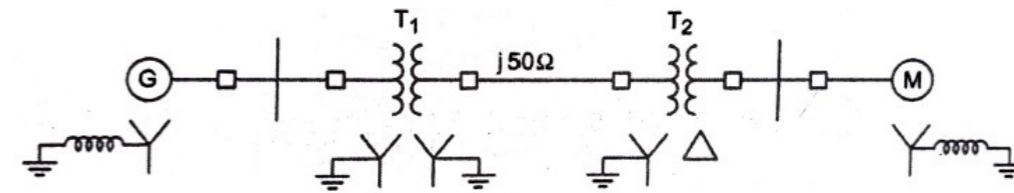


Figure 1

(OR)

- (b) Form Y-bus by singular transformation for the network shown in Figure 2. The impedance data is given in Table 1. Take ① as reference node.

Table 1

Element No.	Self	
	Bus code	Impedance
1	1 – 2 (1)	0.6
2	1 – 3	0.5
3	3 – 4	0.5
4	1 – 2 (2)	0.4
5	2 – 4	0.2

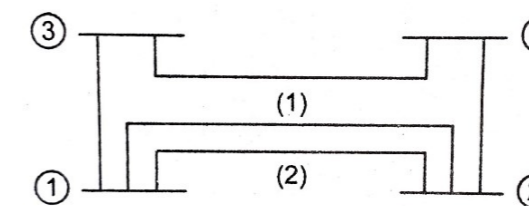


Figure 2

12. (a) Using Gauss-Seidal method, determine bus voltages for the power system shown in Figure 3. Take a base of 100 MVA and  $\alpha=1.1$ .

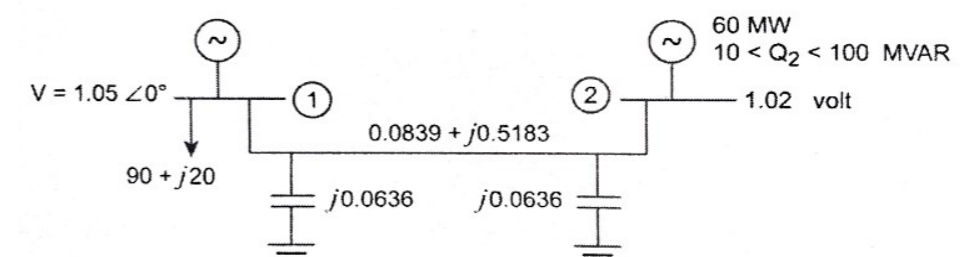


Figure 3

(OR)

- (b) Explain the step by step computational procedure for the Newton-Raphson method of load flow studies. (14) 2 3
13. (a) A 3-phase 5 MVA, 6.6 kV alternator with a reactance of 8% is connected to a feeder of impedance  $(0.12+j0.48) \Omega/\text{phase/km}$  through a step up transformer. The transformer is rated at 3 MVA, 6.6 kV/33 kV and has a reactance of 5%. Determine the fault current supplied by the generator operating under no load with a voltage of 6.9 kV, when a 3-phase symmetrical fault occurs at a point 15 km along the feeder. (14) 3 3

(OR)

- (b) Explain the procedure for making short circuit studies of a large power system network using digital computers. (14) 3 3
14. (a) Determine the fault current and fault MVA for the L-G fault occurs at bus 3 for the power system shown in Figure 4. (14) 4 4

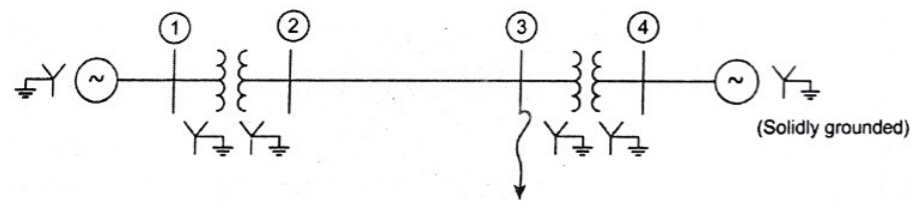


Figure 4

$G_1, G_2$ : 100 MVA; 20 kV;  $X_d''=X_1=X_2=20\%$ ;  $X_0=4\%$   
 $T_1, T_2$ : 100 MVA; 20/345 kV ( $Y_{\Delta} Y_{\Delta}$ )  $X=8\%$   
 Transmission line:  $X_1=X_2=15\%$ ;  $X_0=50\%$

(OR)

- (b) Derive the expression for fault current in Double line-to-ground fault on an unloaded generator in terms of symmetrical components. (14) 4 4
15. (a) (i) Derive the expression for swing equation. (10) 5 3  
 (ii) Enumerate the expressions for critical clearing angle and time. (4) 5 3
- (OR)
- (b) With a neat flow chart explain the steps involved in Runge-Kutta method to determine stability. (14) 5 3

**PART- C(1x 10=10Marks)**

(Q.No.16 is compulsory)

- |  | Marks | CO | RBT LEVEL |
|--|-------|----|-----------|
| 16. The currents flowing in the lines toward a balanced load connected in $\Delta$ are $I_a=10 \angle 0^\circ$ , $I_b=141.4 \angle 225^\circ$ and $I_c=100 \angle 90^\circ$ . Find the symmetrical components of the given line currents and draw phasor diagrams of the positive and negative sequence currents. (10) 4 4 |       |    |           |

\*\*\*\*\*