


Answer **ALL** questions

**PART A - (8 X 2 = 16 marks)**

1. If  $Y_{Bus}$  is symmetric sparse matrix which one of the following is true?
  - (a)  $Z_{Bus}$  is a symmetric sparse matrix
  - (b) Jacobian matrix is a sparse matrix
  - (c)  $Z_{Bus}$  is a Symmetric Full matrix
  - (d) Both b & c
  - (e) Both a & b.
2. When will you consider induction motor in a reactance diagram drawn for fault calculations?
  - (a) during sub-transient conditions
  - (b) during transient conditions
  - (c) during steady state conditions
  - (d) All of the above
3. In which fault zero sequence current cannot be used as fault indicator while designing protection circuits
  - (a) LG fault (b) LL fault (c) LLG fault (d) LLLG fault
4. Which one is true in a transmission line connecting a two bus system?
  - (a)  $SSSL > TSSL > \text{Thermal limit}$
  - (b)  $\text{Thermal limit} > SSSL > TSSL$
  - (c)  $TSSL > SSSL > \text{Thermal limit}$
5. What are the assumptions made while drawing per unit reactance diagram of a power system?
6. Why direct solution of load flow problem is not possible?
7. Define Short circuit Capacity.
8. A power station with 4 generators each 60 MVA, 6 MJ/MVA is in proximity with another power station having 3 generators each 300 MVA, 3.5 MJ/MVA. Calculate the inertia constant of a single equivalent machine for use in stability studies. Assume a base value of 100 MVA.

**PART B - (4 X16 = 64 marks)**

09. (a)

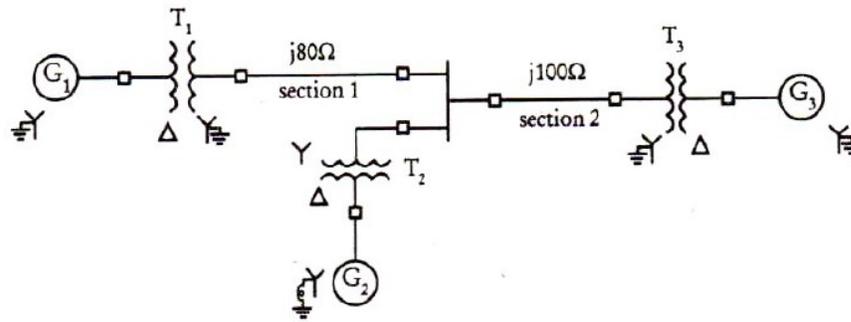

(16)

Figure 1

Figure 1 shows the single line diagram of power system. The generators and transformers are rated as:

Generator G1 = 20 MVA, 13.8 kV,  $X'' = 20\%$

Generator G2 = 30 MVA, 18.0 kV,  $X'' = 20\%$

Generator G3 = 30 MVA, 20.0 kV,  $X'' = 20\%$

Transformer T1 = 25 MVA, 13.8/220 kV,  $X = 10\%$

Transformer T2 = 3 single phase units each rated at 10 MVA, 127/18 kV,  $X = 10\%$

Transformer T3 = 35 MVA, 220/22 kV,  $X = 10\%$

Draw the reactance diagram using a base of 60 MVA and 18 kV on the generator G2 side.

**(OR)**

(b) (i) The three phase ratings of a three winding transformer are:

(8)

Primary Y connected: 66kV, 15 MVA

Secondary Y connected: 13.2 kV, 10MVA

Tertiary Delta connected: 2.3 kV, 5 MVA

Neglecting resistance, the leakage impedances are

$Z_{ps} = 6\%$  on 15 MVA, 66kV base

$Z_{pt} = 7\%$  on 15 MVA, 66kV base

$Z_{st} = 5\%$  on 10 MVA, 13.2kV base

Find the p.u impedances of the Y connected equivalent circuit for a base of 15 MVA, 66kV in the primary circuit.

(ii) For the transmission line with data shown in Table 1, form the bus admittance matrix.

(8)

Table 1

Bus code p-q	Impedance ( $Z_{pq}$ )	Line charging $y_{pq}/2$
1-2	$0.02+j0.04$	$j0.02$
2-3	$0.04+j0.2$	$j0.02$
3-5	$0.15+j0.4$	$j0.025$
3-4	$0.02+j0.06$	$j0.01$
4-5	$0.02+j0.04$	$j0.01$
1-5	$0.08+j0.2$	$j0.02$
2-5	$0.08+j0.2$	$j0.02$

10. (a) (i) Perform Load flow study using Newton Raphson method and determine the power flow solution for the two bus system shown in Figure 2. (12)
- Bus 1 is a slack bus with  $V_1=1.0$  pu at an angle of  $0^\circ$ . The line impedance is  $z_{12}= 0.12+j0.16$  pu on a base of 100 MVA. Obtain the voltage magnitude and phase angle of bus 2. Start with an initial estimate of  $|V_2|=1.0$  p.u and  $\delta_2=0^\circ$ . Perform two iterations.

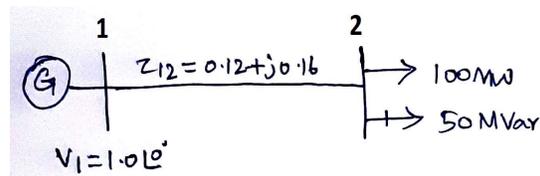


Figure 2

- (ii) The line data, bus data and load flow results are given in Tables 2 and 3. (4)
- Compute the Slack bus power.

Table 2 Line data

Line	Admittance	Half line Charging Admittance
1-2	$1.47-j5.88$	$j0.15$
1-3	$2.94-j11.77$	$j0.07$
2-3	$2.75-j9.17$	$j0.04$

Table 3 Bus data & Load Flow Results

Bus	Bus Voltage	Generation		Load	
		MW	MVAR	MW	MVAR
1 (slack bus)	1.04 at 0°	-	-	0	0
2(PV bus)	1.02 at -3.09°	100	-	50	20
3(PQ bus)	0.93 at -7.01°	0	0	250	150

(OR)

- (b) (i) Figure 3 shows the one-line diagram of a simple three bus power system with generation at buses 1 and 3. The voltage at bus 1 is  $V=1.025$  per unit at an angle of 0 degree. Voltage magnitude at bus 3 is fixed at 1.03 p.u with real power generation of 150 MW. A load consisting of 200 MW and 100 MVar is taken from bus 2. Line impedances are marked in per unit on a 100 MVA base. Line resistances and Line charging susceptances are neglected. Assume Flat voltage profile at load bus. Perform two iterations in Gauss-seidal iterative procedure with acceleration factor =1.045. (12)

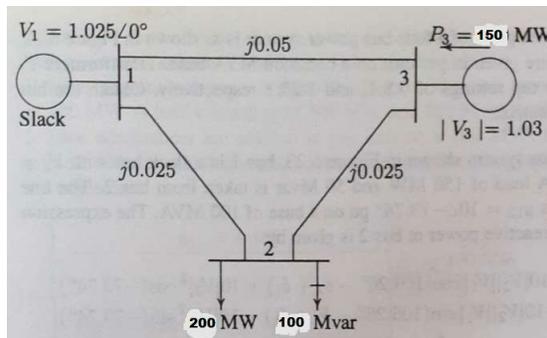


Figure 3

- (ii) How will you model a tap changing transformer for power flow studies? (4)
11. (a) A power system shown in Figure 4 has following specifications: Rating of each machine 1200 KVA, 600 V with  $x_1=x_2=10\%$ ,  $x_0 = 5\%$ . Each three phase transformer is rated 1200 KVA, 600/3300 V (Delta/Star) with leakage reactance of 5%. The reactances of the transmission line are  $x_1 = x_2 = 20\%$  and  $x_0 = 40\%$  on a base of 1200 KVA, 3300 V. The reactances of the neutral grounding reactors are 5% on the KVA and voltage base of the machine. Calculate the fault current for a (a) single line to ground fault (on phase a) (b) Line to Line fault (a-b) (c) Line- Line to (16)

Ground fault occurs at the midpoint of transmission line.



Figure 4

(OR)

- (b) (i) A 50 MVA, 11kV three phase synchronous generators was subjected to different types of faults. The fault currents are as follows. LG fault: 4200 A, LL fault: 2600A, LLLG fault: 2000A. The generator neutral is solidly grounded. Find the per unit values of the three sequence reactances of generator. (8)
- (ii) Two generating stations with short circuit capacities of 1500 MVA, 1000 MVA respectively are interconnected by means of a reactor. Determine the value of the reactor to limit the short circuit capacity of station 1 to be 1600 MVA. (8)

12. (a) A power system with p.u reactance values is shown in Figure 5. Form  $Z_{bus}$  using  $Z_{bus}$  building algorithm. For a solid three phase fault occurring on bus 3, Calculate the Fault current ( $I^f$ ) and Voltage at buses 1 & 2 during fault ( $V_1^f$  and  $V_2^f$ ). Assume pre-fault voltages to be 1p.u and ignore pre-fault currents. (16)

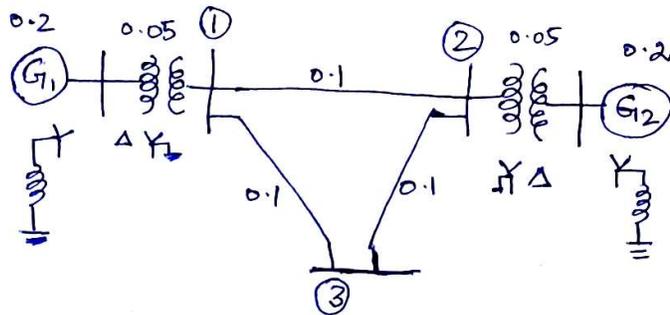


Figure 5

(OR)

- (b) (i) Figure 6 represents a generator supplying power to infinite bus system. The generator is supplying 1.0 pu power with terminal voltage of 1.08 pu. Generator transient reactance is 0.12 pu . Transformer reactance is 0.09 pu. Line reactance is 0.18 pu. A 3 phase fault occurs at the terminals of the generator and the fault gets cleared after 1.25 cycle without any CB opening . (14)

**Q. Code: 337784**

Compute swing curve upto  $t = 0.05$  sec . Use Ruge-kutta method .  $H=5$ pu.

Infinite bus voltage may be assumed to be  $(1 + j0)$  pu and frequency as 50 HZ.

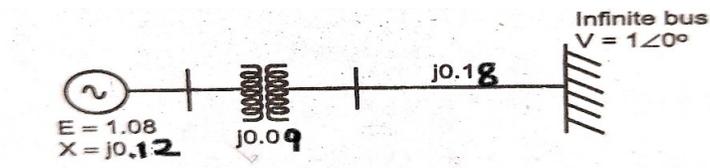


Figure 6

- (ii) Draw power angle curve for a three phase fault with subsequent clearing in a power system in which a generator is connected to a infinite bus bar through a double circuited transmission line and show the accelerating and decelerating areas. (2)