

Reg. No.

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2023

Second Semester

CS22202 – DIGITAL PRINCIPLES AND SYSTEM DESIGN*(Computer Science and Engineering)***(Regulation 2022)****TIME: 3 HOURS****MAX. MARKS: 100**

| COURSE OUTCOMES | STATEMENT | RBT LEVEL |
|-----------------|---|-----------|
| CO 1 | Students will be able to learn the different types of number systems and simplification of Boolean functions | 4 |
| CO 2 | Students will be able to understand various logic gates and their usage | 2 |
| CO 3 | Students will be able to study, analyze and design various combinational circuits and its implementation using VHDL | 4 |
| CO 4 | Students will be able to understand the different type of memory and their structures | 2 |
| CO 5 | Students will be able to study, analyze of RTL notation register operations in a clocked sequential circuit | 4 |

PART- A (20 x 2 = 40 Marks)*(Answer all Questions)*

| | CO | RBT LEVEL |
|---|----|-----------|
| 1. Write the classification of binary codes. | 1 | 2 |
| 2. Represent a OR gate using NAND gate. | 1 | 3 |
| 3. What is the use of Don't care conditions? | 1 | 2 |
| 4. What is propagation delay? | 1 | 2 |
| 5. Draw 1:8 demultiplexer using two 1:4 Demultiplexer. | 2 | 3 |
| 6. What is magnitude comparator? | 2 | 1 |
| 7. How full adder is obtained from two half adders? | 2 | 3 |
| 8. Draw the circuit for 2-to-1 multiplexer. | 2 | 2 |
| 9. State the difference between latches and flipflops. | 3 | 2 |
| 10. Write any two applications of shift register. | 3 | 2 |
| 11. What is meant by edge triggered flip flops? | 3 | 2 |
| 12. Draw the excitation table of JK- flip flop. | 3 | 2 |
| 13. What are error detecting codes? Give examples. | 4 | 2 |
| 14. Draw the basic configuration of PROM. | 4 | 2 |
| 15. How many check bits are required for single bit error detection and correction? | 4 | 3 |
| 16. State the difference EPROM and EEPROM. | 4 | 2 |
| 17. List any two HDL operators and their symbols used in RTL design. | 5 | 2 |
| 18. Write a short note on register transfer level. | 5 | 2 |
| 19. Draw a block diagram for Sequential Binary Multiplier. | 5 | 2 |
| 20. Differentiate LOGICAL AND and BITWISE AND operators. | 5 | 2 |

PART- B (5 x 10 = 50 Marks)

| | | Marks | CO | RBT LEVEL |
|----------------|---|-------------|----------|--------------|
| 21. (a) | (i) Simplify the following Boolean expression to a minimum number of literals. $A'B' + A'C'D' + A'B'D + A'B'CD'$. | (5) | 1 | 4 |
| | (ii) Convert the given expression in canonical SOP form $Y = AC+AB+BC$. | (5) | 1 | 4 |
| | (OR) | | | |
| (b) | State and Prove the Demorgan's theorem and Consensus theorem. | (10) | 1 | 4 |
| 22. (a) | Design a combinational circuit to convert binary to gray code. | (10) | 2 | 3 |
| | (OR) | | | |
| (b) | With neat diagram explain the 4-bit adder with carry look ahead. | (10) | 2 | 3 |
| 23. (a) | With logic sketch explain the universal shift register as a storage device. | (10) | 3 | 3 |
| | (OR) | | | |
| (b) | Implement JK flip flop using D flip flop. | (10) | 3 | 3 |
| 24. (a) | Explain in detail about the Programmable Logic Array, Programmable Programmable Logic. | (10) | 4 | 4 |
| | (OR) | | | |
| (b) | Explain about error detection and correction using hamming codes. | (10) | 4 | 2 |
| 25. (a) | Explain in detail about the Algorithmic State Machine chart. | (10) | 5 | 2 |
| | (OR) | | | |
| (b) | Explain how a hardware description language includes operators that correspond to the register transfer operations of a digital system? | (10) | 5 | 4 |

PART- C (1 x 10 = 10 Marks)

(Q.No.26 is compulsory)

| | | Marks | CO | RBT LEVEL |
|------------|--|-------------|----------|--------------|
| 26. | Design a full subtractor and derive expression for difference and borrow. Realize the circuit using gates. | (10) | 2 | 5 |
