

Reg. No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2023**

Second Semester

**EC22202 – CIRCUIT THEORY**

(ELECTRONICS AND COMMUNICATION ENGINEERING)

(Regulation 2022)

TIME: 2 HOURS

MAX. MARKS: 60


COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Apply suitable network theorems and analyze AC and DC circuits.	3
CO 2	Infer the phenomenon of series and parallel resonance in electrical circuits and understand the effect of magnetic coupling between windings	2
CO 3	Analyze the transient response for any RC, RL and RLC circuits.	4
CO 4	Evaluate the two port network parameters.	5
CO 5	Sketch the various network topologies.	4

**PART- A (10 x 2 = 20 Marks)**

(Answer all Questions)

1. Identify the current flowing through R3 resistor in the below Circuit.

CO	RBT LEVEL
1	3

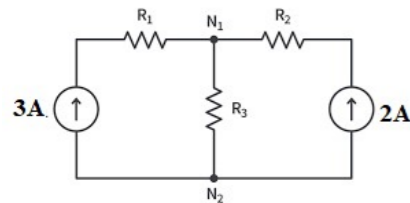


- |     |   |   |   |
|-----|---|---|---|
| 2.  | Construct a series RL circuit if the supply voltage is $v(t) = 10\cos(2t+600)$ V, $R = 2\Omega$ and $L = 5H$ . Find current in the circuit?     | 1 | 3 |
| 3.  | Infer the coefficient of coupling for the two coupled coils have a self-inductances 37.5 mH and 193 mH, with the mutual inductance of 63.75 mH. | 2 | 2 |
| 4.  | Construct an RLC series circuit has $R = 10\Omega$ , $L = 2H$ . What value of capacitance will make the circuit critically damped?              | 3 | 3 |
| 5.  | Outline the frequency response of a single tuned circuits.  | 3 | 2 |
| 6.  | Summarize the significance of the ABCD parameters in interconnection of two-port networks?  | 4 | 2 |
| 7.  | Make use of the two port network, $Z_{11} = 100\Omega$ , $Z_{21} = 120\Omega$ , $Z_{12} = 120\Omega$ , $Z_{22} = 50\Omega$ . Find Y parameters. | 4 | 3 |
| 8.  | Summarize the difference between a T-network and a $\pi$ -network in two-port circuits?   | 4 | 2 |
| 9.  | Develop link current and tie set matrix   | 5 | 3 |
| 10. | Summarize the basic mesh analysis procedure.  | 5 | 2 |

**PART- B (3 x 10 = 30 Marks)**


Marks	CO	RBT LEVEL
-------	----	-----------

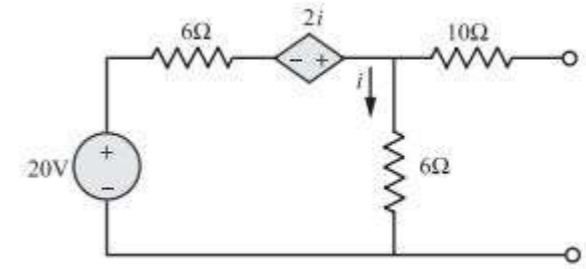11. (a) Analyze the Thevenin's equivalent for the circuit shown in Fig. with respect to terminals? (10) 1 4




(OR)

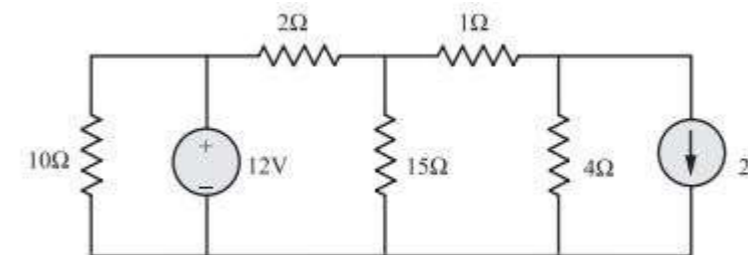(b) Examine the current through 15ohm resistor using superposition theorem (10) 1 4



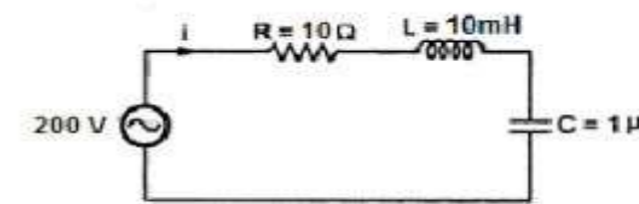12. (a) Build a series RLC circuit with  $R = 10\Omega$ ,  $L = 10mH$  and  $C = 1\mu F$  has an applied voltage of 200 V at resonance frequency. Calculate i) resonant frequency ii) current and voltage across the elements at resonance iii) Quality factor iv) Bandwidth of the circuit. (10) 2 3




$R = 10\Omega$ ,  $L = 10\text{ mH}$ ,  $C = 1\mu F$ ,  $V = 200V$

(OR)


(b) Build the expression for coefficient of coupling in terms of mutual and self-inductances of the coils (10) 2 3

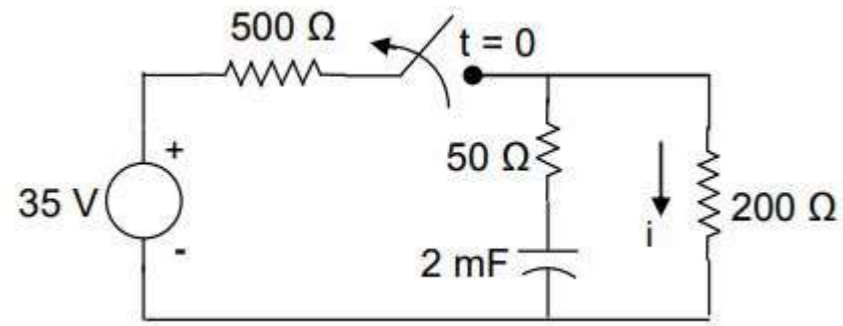13. (a) Decide the circuit's current  $i(t)$  at  $t > 0$ . The switch was in closed position for a long time. It is opened at time  $t = 0$  (10) 3 5



(OR)

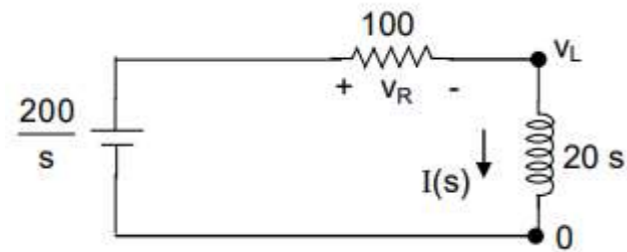
- (b) Evaluate the following parameters, when Initially relaxed series RL circuit with  $R = 100 \Omega$  and  $L = 20 \text{ H}$  has dc voltage of 200 V applied at time  $t = 0$ . (10) 3 5
- (a) the equation for current and voltages across different elements
  - (b) the current at time  $t = 0.5 \text{ s}$  and  $1.0 \text{ s}$
  - (c) the time at which the voltages across the resistor and inductor are equal.



**PART- C (1 x 10 = 10 Marks)**  
(Q.No.14 is compulsory)

14. Make use of the circuit, draw the graph, one tree and its co-tree.

Marks	CO	RBT LEVEL
(10)	5	3

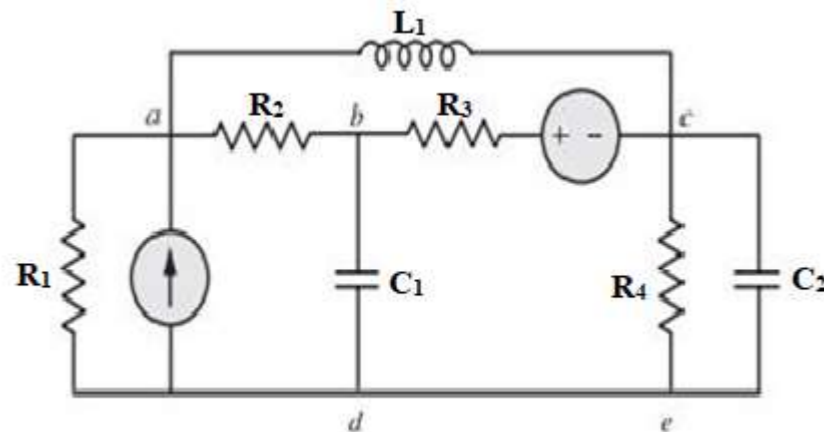

\*\*\*\*\*